



TARGET : NEET (UG) 2024

Course : SARANSH (Youtube Live CRASH COURSE)

PHYSICS

DPP


DAILY PRACTICE PROBLEMS

DPP NO. 1

PHYSICS: CURRENT ELECTRICITY

DPP No. : 1

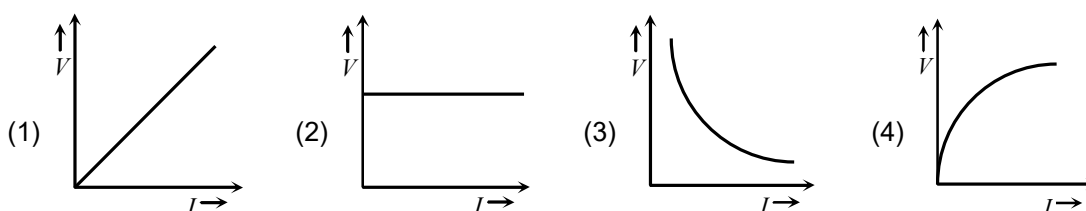1. Which of the adjoining graphs represents *ohmic* resistance



2. Drift velocity v_d varies with the intensity of electric field as per the relation

(1) $v_d \propto E$ (2) $v_d \propto \frac{1}{E}$ (3) $v_d = \text{constant}$ (4) $v_d \propto E^2$

3. A car has a fresh battery of e.m.f. 12 V and internal resistance of 0.05 Ω . If the starter motor draws a current of 90 A, the terminal voltage when the starter is on will be

(1) 12 V (2) 10.5 V (3) 8.5 V (4) 7.5 V


4. If nearly 10^5 C liberate 1 g equivalent of aluminium, then the amount of aluminium (equivalent weight 9) deposited through electrolysis in 20 min by a current of 50 amp will be :

(1) 0.6 g (2) 0.09 g (3) 5.4 g (4) 10.8 g

5. The drift velocity of electrons in a conducting wire is of the order of 1mm/s, yet the bulb glows very quickly after the switch is put on because


- (1) The random speed of electrons is very high, of the order of 10^6 m/s
 (2) The electrons transfer their energy very quickly through collisions
 (3) Electric field is set up in the wire very quickly, producing a current through each cross section, almost instantaneously
 (4) All of above

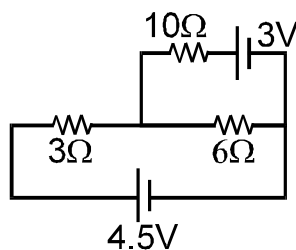6. A piece of copper and another of germanium are cooled from room temperature to 80 K. The resistance of :
- (1) each of the them increases
 - (2) each of them decreases
 - (3) copper increases and germanium decreases
 - (4) copper decreases and germanium increases
7. In an electric circuit containing a battery, the positive charge inside the battery
- (1) always goes from the positive terminal to the negative terminal
 - (2) may go from the positive terminal to the negative terminal
 - (3) always goes from the negative terminal to the positive terminal
 - (4) does not move.
8. Find the current through the $10\ \Omega$ resistor shown in figure




- (1) zero (2) 1 A (3) 2A (4) 5 A

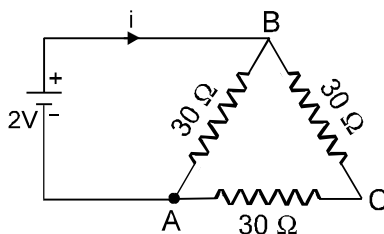9. The current i in the circuit of figure is -



- (1) $\frac{1}{45}$ amp. (2) $\frac{1}{15}$ amp. (3) $\frac{1}{10}$ amp. (4) $\frac{1}{5}$ amp.

10. The reading of voltmeter is

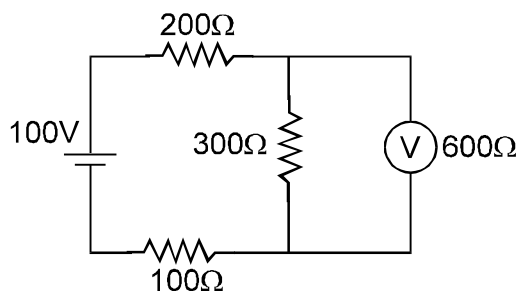

- (1) 50V (2) 60 V (3) 40V (4) 80 V